# **Project board GFCI**

Program: Electrician Technician

Course: EL190

**Objective:** Under the supervision of your instructor, you should be able to do the following:

- Wire a GFCI for protection of only itself and for protection of other devices.
- Explain how a 3-way switch works
- Explain how a single pole switch works
- Explain how to make a duplex receptacle into a ½ hot or switched outlet.
- Install a basic light fixture

Lab Equipment: Project Boards

# **Required Tools:**

- 1 Flathead screwdriver
- 1 Pair of strippers
- 1 Phillips's screwdriver
- 1 Plug-in tester

Materials: (Includes project boards material)

- 2' 14 AWG THHN black
- 2' 14 AWG THHN white
- 2' 14 AWG THHN green
- 2' 14 AWG THHN red
- 2' 14 AWG THHN blue
- 6 4S boxes no brackets
- 12 ½" EMT set screw connectors
- 40" ½" EMT pipe
- 1 24" x 16" plywood
- 12 ½" screws
- 6 Green ground screws
- 15 Red wire nuts
- 1 GFCI receptacle
- 2 single pole switch 2 3-way switches
- 1 duplex receptacle
- 2 keyless fixtures
- 2 lamps
- Power cord

# Safety (PPE):

- Safety glasses/goggles
- Hard hat

#### Resources:

N/A

Required Time: Two days

#### **Shop Maintenance:**


- All work will cease 20 minutes prior to the end of class.
- All work areas must be cleaned.
- Tools and equipment must be cleaned and returned to the designated areas (cage, tool room, cabinets etc.)
- Any broken or missing tools must be reported immediately.
- Tools and equipment are students' responsibility

#### Procedure:

- Wire from a power, to a GFCI, to a switch, to a keyless light fixture (operated by the switch), on the LINE side.
- 2. Wire from a power, to a GFCI, to a switch, to a keyless light fixture (operated by the switch), on the LOAD side.
- 3. Wire from a power cord, to a GFCI, to a duplex receptacle to a switch to a keyless light fixture (operated by the switch), on the LINE side.
- 4. Wire from a power cord, to a GFCI, to a duplex receptacle, to a switch, to a keyless light fixture (operated by the switch), on the LOAD side.
- 5. Wire from a power cord, to a GFCI, to a 3-way switch to a keyless fixture to another 3-way switch, which operates the light on the LINE side.
- 6. Wire from a power cord, to a GFCI, to a 3-way switch to a keyless fixture to another 3-way switch, which operates the light on the LOAD side.
- 7. Wire from a power cord, to a GFCI, to a Duplex receptacle (1/2 hot), to a switch, to a keyless light fixture, on the LINE side. The switch operates both the ½ hot and the light.
- 8. Wire from a power cord, to a GFCI, to a Duplex receptacle (1/2 hot), to a switch, to a keyless light fixture, on the LOAD side. The switch operates both the ½ hot and the light.
- 9. Wire from a power cord, to a GFCI, to a duplex ½ hot receptacle, to a switch, to a 3-way switch, to a keyless light fixture, to another 3-way switch, on the LINE side. The switch operates the ½ hot and the 3-way switches operate the keyless light fixture.
- 10. Wire from a power cord, to a GFCI, to a duplex ½ hot receptacle, to a switch, to a 3-way switch, to a keyless light fixture, to another 3-way switch, on the LOAD side. The switch operates the ½ hot and the 3-way switches operate the keyless light fixture.
- 11. Wire from a power cord, to a GFCI, to a switch from the LINE side to a light fixture, (operated by the switch). Then from the GFCI, wire to a switch from the LOAD side to a light fixture, (operated by the switch).

# **UEI COLLEGE • UNITED EDUCATION INSTITUTE**

# **Project Board**

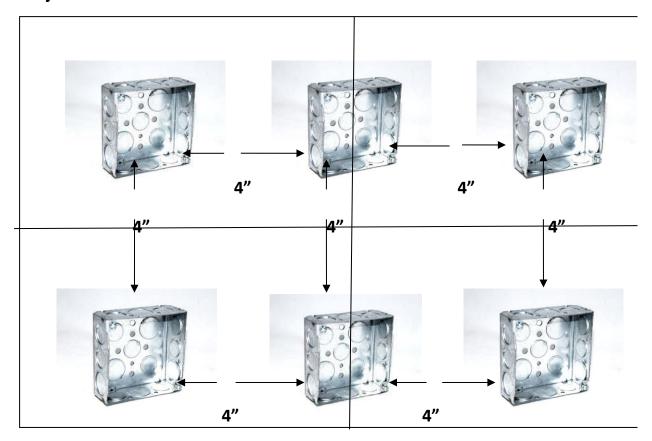

### Example for number 1:

- First box (Top Left) Power cord coming in from the left side, GFCI device will be installed
- Second box (Top Middle) One single pole switch, (Line side of GFCI), will be installed
- Third box (Top Right) One keyless light fixture will be installed operated by the switch in box 2

### Example for Number 11:

- First box (Top Left) Power cord coming in from the left side, GFCI device will be installed
- Second box (Top Middle) One single pole switch, (Line side of GFCI), will be installed
- Third box (Top Right) One keyless light fixture will be installed operated by the switch in box 2
- Fourth box (Bottom Left) One single pole switch, (Load side of GFCI), will be installed
- Fifth box (Bottom Middle) One keyless light fixture will be installed operated by the switch in box 2