Install and Connect a Branch Circuit in a Panelboard

Program: Electrician Technician

Course: EL140 – Residential Applications

Objectives: Under the supervision of your instructor, you should be able to do the following:

- Select the proper wiring methods for several types of residences
- Explain the purpose of ground fault circuit interrupters and tell where they must be installed
- Explain how wiring devices are selected and installed

Lab Equipment:

N/A

Required Tools:

- 1 Screwdriver set
- 1 Channel Locks pliers
- 1 Torpedo level
- 1 Hammer
- 1 Pair of Diagonal cutters
- 1 Pair of Wire strippers

Materials:

- 10' 14/2 AWG NM cable with ground (Romex®)
- 1 1/2" NM cable fittings, 2 screw connectors
- 1 Single gang plastic side nail box
- 1 Duplex receptacle
- 1 Duplex receptacle plate cover
- 1 Single-pole, 15 ampere GFCI circuit breaker (compatible with branch circuit panel)
- 2 4 NM cable staples as required

Safety (PPE):

- Safety glasses
- Hard hat if working in bays

Resources- N/A

Time Required: 120 Minutes

Shop Maintenance:



UEI COLLEGE . UNITED EDUCATION INSTITUTE

- All work will cease 20 minutes prior to the end of class.
- All work areas must be cleaned.
- Tools and equipment must be cleaned and returned to the designated areas (cage, tool room, cabinets etc.)
- Any broken or missing tools must be reported immediately.
- Tools and equipment are the student's responsibility

Procedures: (Eye protection must always be worn)

This performance project requires you to select and install a surface-mounted NEMA 1 branch circuit panel enclosure and branch circuit conductors supplying a duplex receptacle installed in a surface-mounted handy box. 14/2 AWG NM cable with ground will be used as the branch circuit conductors. The circuit will be protected by a 15-ampere, single-pole GFCI circuit breaker installed in the branch circuit panel.

- 1. Select and install a branch circuit panel enclosure and handy box on the lab board.
- 2. Prepare the panel enclosure with a 1/2" NM connector
- 3. Mount the single gang box
- 4. Install 14/2 AWG NM cable with ground between the branch circuit panel enclosure and the single gang box, securing the NM cable according to the requirements of **NEC Article 334**.
- 5. Cut, strip, and prepare the NM cable conductors at the outlet end to receive a duplex receptacle.
- 6. Install a duplex receptacle and cover plate at the outlet.
- 7. Cut, strip, and prepare the NM cable conductors at the panel end for termination.
- 8. Connect the circuit's equipment grounding conductor to the grounding bus in the panel.
- 9. Select and install a single-pole, 15-ampere GFCI circuit breaker in the panel enclosure (*Figure 1*). Turn the circuit breaker to the OFF position.
- 10. Terminate the neutral pigtail from the GFCI circuit breaker on the neutral bus bar in the panel.
- 11. Terminate the grounded (neutral) circuit conductor on the GFCI circuit breaker.
- 12. Terminate the ungrounded circuit conductor on the GFCI circuit breaker.
- 13. Have your instructor check your work.

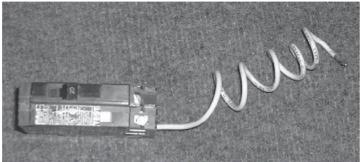


Figure 1 ■ Single-Pole, 20-Ampere GFCI Circuit Breaker